

Assignment 2

- Using the properties of a general Boolean Algebra (whose elements are not only 0 and 1), reduce the following expressions into a minimum sum of products form:

(a) $x'y'z' + x'y'z + x'yz + xy'z + xyz + xyz'$

(b) $a'b'c' + a'bc' + a'bc + ab'c + abc' + abc$

- Consider a Boolean algebra with $S = \{0, 1\}$. Let $f : S^3 \rightarrow S$ whose values are given as $f(i) = 0$ for $i = 1, 2, 5, 7$ and $f(i) = 1$ for $i = 0, 3, 4, 6$.

- Derive the Boolean function in sum of minterms canonical form.
- Derive the Boolean function in product of maxterms canonical form.
- Derive the Boolean function in Reed-Muller canonical form.

- Show a block diagram of a system using AND, OR, and NOT gates to implement the following function. Assume that the variables are only uncomplemented. Do not manipulate the algebra.

$$F = (A(B + C)' + BDE)(A' + CE)$$

- Show a block diagram corresponding to the following expression using only NAND gates. Assume all inputs are available both uncomplemented and complemented. There might be a need to manipulate the function to simplify the algebra.

$$f = b(c'd + c'e') + (a + ce)(a' + b'd')$$

- Show a block diagram corresponding to the following expression using only NOR gates. Assume all inputs are available both uncomplemented and complemented. There might be a need to manipulate the function to simplify the algebra.

$$g = \{a'b' + a(c + d)\}(b + d')$$

- A minority function has an output value of 1 if there are less 1's than 0's on its inputs. The output is 0 otherwise. Consider the design of the four input minority function.

- Tabulate the truth table for the four input minority function.
- Derive the output Boolean function in sum of minterms form (SOM) and product of maxterms (POM) form.
- Optimize the output Boolean function in sum of products form (SOP) and product of sums form (POS) using the axioms of a general Boolean Algebra.