

## COMP 249 Logic Circuits

Due: 26-October-2009

Monday 23:55

### Assignment 3

1. For each of the following functions, find all prime implicants using the Quine-McCluskey method:
  - (a)  $f(a, b, c) = \Sigma m(1, 2, 3, 6, 7)$
  - (b)  $g(w, x, y, z) = \Sigma m(2, 3, 6, 7, 8, 10, 11, 12, 13, 15)$
  - (c)  $h(p, q, r, s) = \Sigma m(5, 7, 9, 11, 13, 14), \Sigma d(2, 6, 10, 12, 15)$
2. Consider the Boolean functions given in Problem 1, and using Quine-McCluskey method, minimize each function in
  - (a) Sum of Products (SOP) form
  - (b) Product of Sums (POS) form
3. Consider the following Boolean functions:
  - (a)  $F(A, B, C, D) = AD + AB + A'CD' + B'CD + A'BC'D'$
  - (b)  $g(w, x, y, z) = (w + y' + z')(x' + y + z')(w' + y')(w' + x' + y + z)(w' + z')(x' + y' + z)$

Using Karnaugh method, minimize these Boolean functions in both sum of products (SOP) form and product of sums (POS) form.

4. Design a circuit with output  $f$  and inputs  $x_1, x_0, y_1$ , and  $y_0$ . Let  $X = x_1x_0$  be a number, where the possible values of  $X$ , namely, 00, 01, 10, and 11, represent the four numbers 0, 1, 2, and 3, respectively. Similarly, let  $Y = y_1y_0$  represent another number with four possible values. The output  $f$  should be 1 if the numbers represented by  $X$  and  $Y$  are equal. Otherwise,  $f$  should be 0.
  - (a) Show the truth table for  $f$ .
  - (b) Using the Quine-McCluskey method, synthesize the simplest possible product of sums (POS) expression for  $f$ .
  - (c) Using Karnaugh method, optimize the Boolean function in sum of products form (SOP).
  - (d) Draw the logic circuit implementation of the Boolean function as a two-level NOR circuit and a two-level NAND circuit.